

THE HONG KONG UNIVERSITY OF SCIENCE AND TECHNOLOGY
Department of Electronic and Computer Engineering
ELEC 1100

Laboratory 6: Assembly of the Robot Car (4%)

A) Objectives:

- By applying all techniques learned in the previous labs, design and complete the control circuit of the robot vehicle so that it can track along a racing track.

B) Hardware and Software:

- Robot Car Kit with tools (with line sensors)
- Nano-Board (Arduino compatible) and open-source **Arduino Software (IDE 1.8.19)**

C) Experimental Procedures:

Experiment 1: Build the Robot Car (~40min)



Step 1: Download the “**Robot Car Guide_Full Assembly**” file from your Canvas lab page. A **demonstration video** for the full assembly is also available on Canvas for your reference.

Step 2: Assemble the full version of your Robot Car following the guide or demo video.

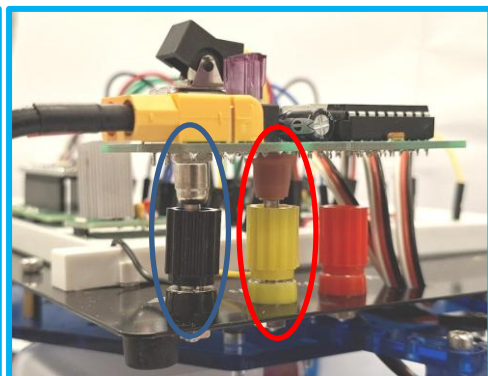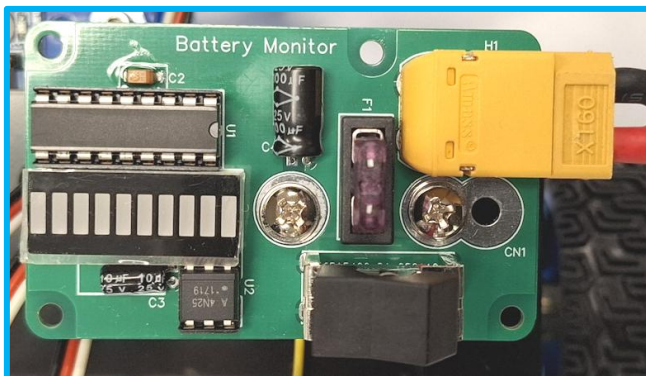**** **TA Check 1: Show the Robot Car to your TA** ****

Experiment 2: Confirm the Voltage on the Breadboard (~20 mins)

Step 1: Connect the **~12V battery** to the battery monitor. Insert the battery monitor into the breadboard's power socket, then connect its **positive** output to the **12V bus** and its **negative** output to the **GND bus**, as you set up in Lab 4 or Lab 5.



Notice

- This **12V** battery is the power source for the complete circuit on your breadboard.
- Anywhere a **5V** is needed it should be connected to the **LM7805** output through your breadboard **5V-bus**.

Step 2: Press the **black button** on the battery monitor to turn it on. Then measure the voltage at each pin listed in the table below to verify your circuit connections.

Note: During the project period, you will need to refer to the project “**Supplementary**” file to charge the battery regularly and properly to power your robot car system.

However, do **NOT**** charge your car battery in Lab 6 class.**

It takes more than 8 hours to fully charge a low energy level battery.


For Lab 6, you may use the DC power supply to provide 12V if the car battery is low.

**** TA Check 2: Demo to your TA that the voltage measurements on your breadboard match with the table below to confirm your Lab 5 circuit connections ****

LM7805 Regulator		L293 Motor Driver		74HC14 Inverter		Nano-board
V _{in}	V _{out}	Pin 8	Pin 16	Pin 7	Pin 14	+5V terminal
12V	5V	12V	5V	0V	5V	5V


Experiment 3: The measurements of Car Sensors (~20 min)

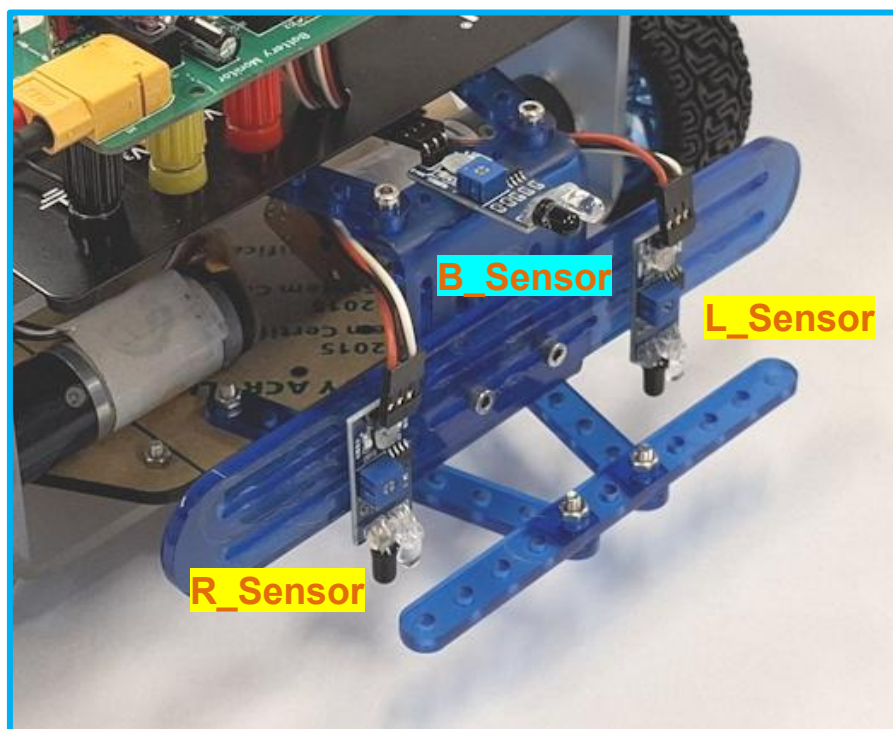Step 1: Install the three sensors on your car as shown in the demo video and the photo below. One sensor will serve as the **bumper sensor (B_Sensor)** to start the robot car. The other two sensors—the **left (L_Sensor)** and **right (R_Sensor)**—should face downward to detect the racing track.



Step 2: Power and ground each sensor to the **5V-bus** or **GND-bus** on your breadboard and connect sensor outputs (from sensor “OUT” pin) to the **Nano-board** as shown below

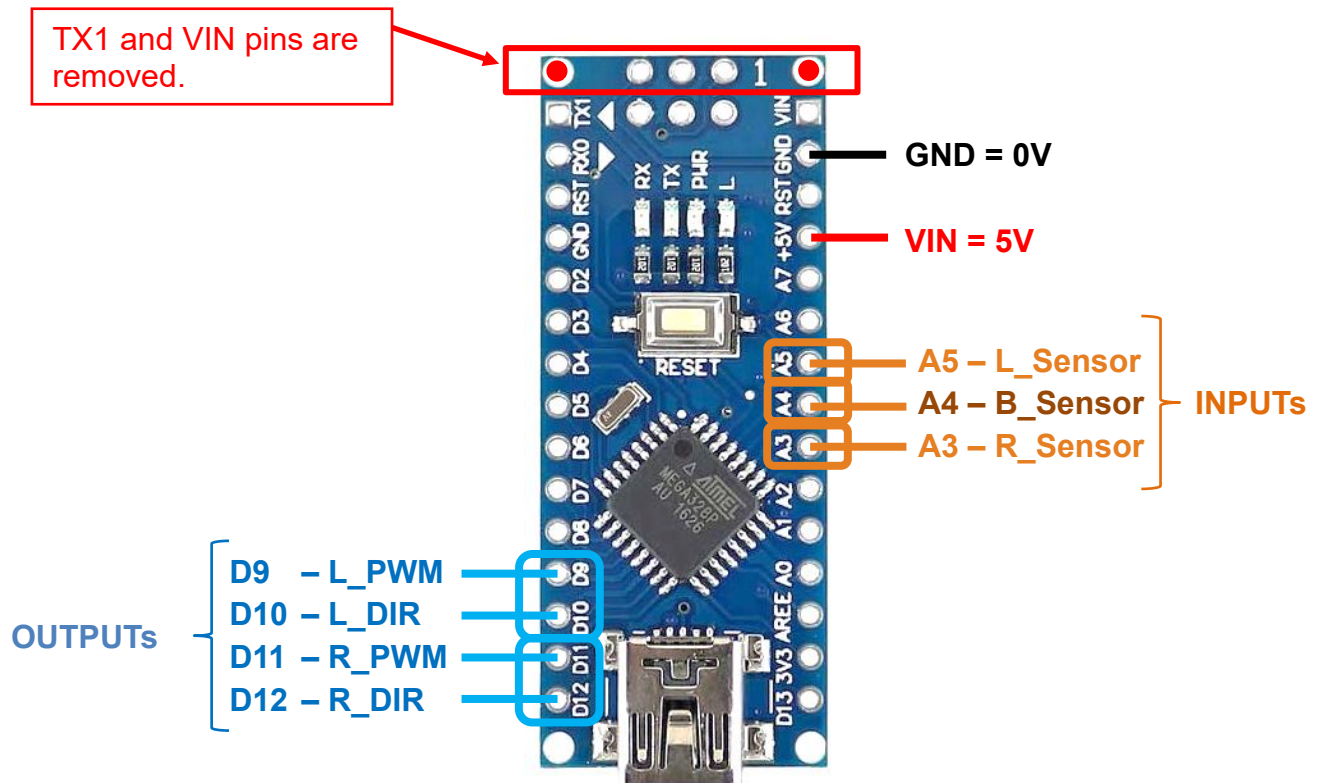You may refer to the **example breadboard layout** provided in the **tutorial notes**.



Step 3: **Disconnect the two motors from your breadboard for now.**

Step 4: Examine your car sensors one by one:

- Bumper sensor: put your hand (or a white paper) in front of the sensor, the external LED is “ON” when seeing “white” and could be turned “OFF” when not seeing “white”.
- Left and right sensors: move your car across a white line on the black mat, the external LED is “ON” when seeing “white” and “OFF” when seeing “black”.

If not, do the followings:

- modify the **sensitivity of the sensor** by adjusting the variable resistor using a screwdriver.
- adjust the **sensor height** (the height of your **Car Front Bar**) from the racing track.

TA Check 3: Show demo to your TA that:

- (1) The bumper sensor can respond to when your hand (or white paper) is in front of it.
- (2) Each of the left & right sensors can differentiate the white line from the black mat.


Experiment 4: Robot Car Motion Control (~20 min)

In this experiment, you are going to program the Nano-board to control your robot car to move along a racing track.

The racing track is a white line on a black mat as shown below.

➤ **Your tasks are to let the robot car achieve:**

Task No.	Tasks
1	After power on, car wheels should be STOP after board initialization .
2	Put the car at the start position with all front-bar sensors ON the horizontal START white line . The car should still be at STOP state.
3	The bumper sensor is triggered to start the robot car. Follow the straight line until reaching the 'T' junction.
4	Navigate the "go left" turning at the junction.

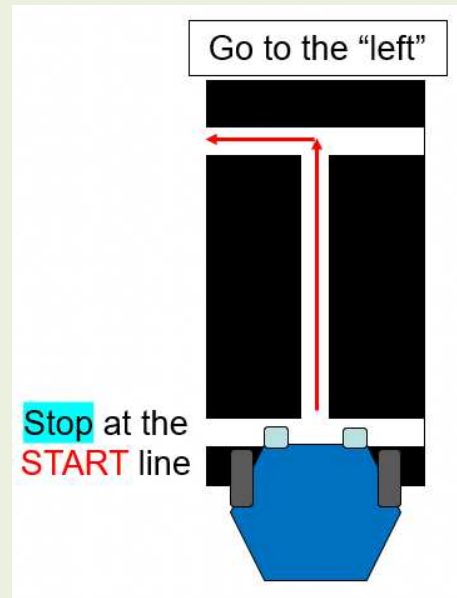

Before the coding work, you are required to power OFF your circuit and double-check your breadboard connection.

Step 1: Confirm that the **B_Sensor** (sensor "OUT" pin) is connected to the Nano-board **A4**.


Step 2: Confirm that the **L_Sensor** and **R_Sensor** (sensor "OUT" pin) are connected to the Nano-board **A5** and **A3**, respectively.

You may refer to the circuit diagram on the next page to check the connections between the Nano-board and the L293 motor driver.

Step 3: Confirm that from the **Nano-board D9** and **D10**, the **L_PWM** and **L_DIR** are connected to the **L293 pin 1** and **pin 2**, respectively.

Step 4: Confirm that from the **Nano-board D11** and **D12**, the **R_PWM** and **R_DIR** are connected to the **L293 pin 9** and **pin 10**, respectively.

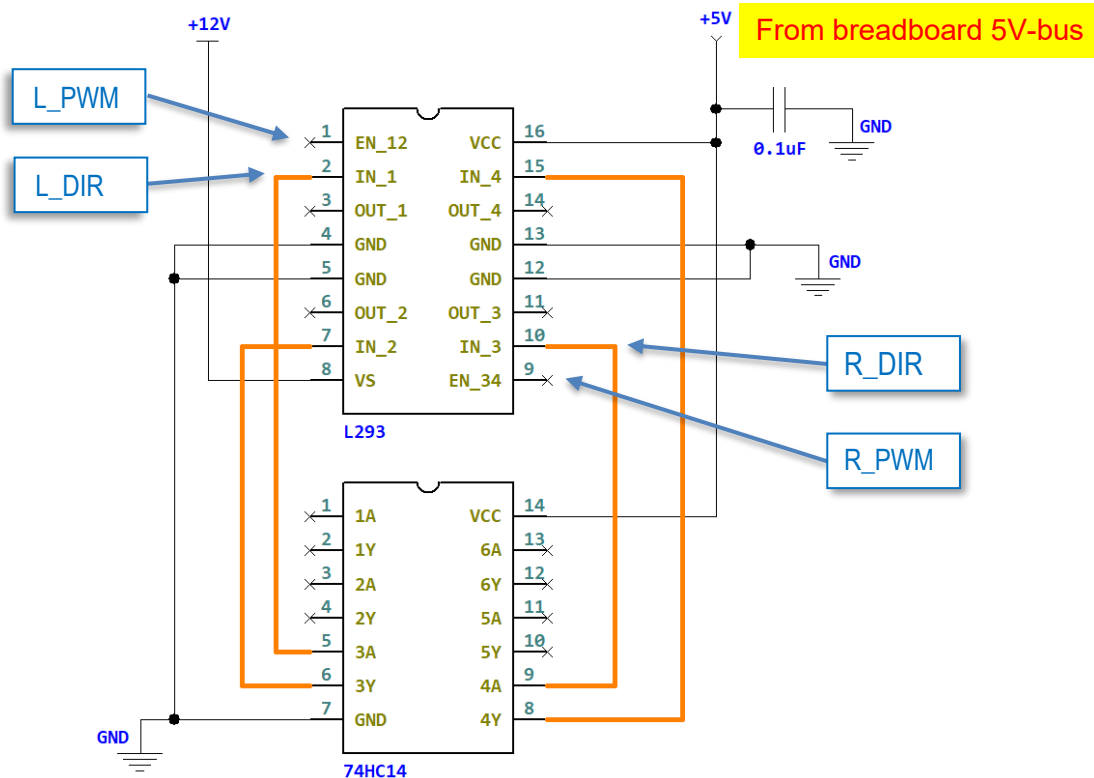Step 5: After you are done checking, plug the car's left motor headers into the breadboard rows connected to the L293 pin 3 (+), 4, 5, and 6 (-), and plug the car's right motor headers into the breadboard rows connected to L293 pin 14 (+), 13, 12 and 11(-).



Step 6: **Download** the “lab_06_logic” Arduino sketch program from your Canvas lab page.

It is highly recommended to use [Arduino IDE 1.8.19](#) for reliable compiling performance.

The most recent versions may not align well with your laptop due to various compatibility issues.

Step 7: Replace the question marks (“???”) with the corresponding **PWM** and **DIR** values required for the robot car to complete the Lab 6 tasks (**Tasks 1–4** on page 4).

You may refer to the **example coding solution** provided in the [tutorial notes](#).

Step 8: **Take away the Nano-board from the IC socket** and upload your complete code using the USB cable.

DO NOT do uploading when the Nano board is still in the IC socket.

This may damage the Nano-board because of high current load on pins.

Step 9: Put the Nano-board back into the IC socket after uploading the sketch.

**** **TA Check 4: Demo to your TA the successfulness of Tasks 1-4 on the small mat** ****

You have learned all the basics, and you are now ready for your project!