

The Hong Kong University of Science and Technology
Department of Electronic and Computer Engineering

ELEC2400 **ELECTRONIC CIRCUITS** FALL 2026-27

Lab Section No. : _____ Date : _____

Name : _____ Student Number : _____

LAB 2 – PSpice Circuit Simulation

Q1. What is the simulated current I_1? _____

Q2. What is the simulated current I_2? _____

Q3. What is the simulated voltage V_1? _____

Q4. What is the simulated current I_3? _____

Q5. What is the simulated voltage V_2? _____

Q6. What is the simulated Vab? _____

Q7. What is the simulated V_{OC}? _____

Q8. What is the simulated I_{SC}? _____

Q9. What is the calculated R_{eq}? _____

Q10. What is the calculated I_O? _____

Q11. What is the calculated V_{ab} ? _____

Q12. What is the simulated V_4? _____

Q13. What is the equation of $v_o(t)$? _____

Q14. What is the maximum of v_o? _____

Q15. What is the resonant frequency? _____

Q16. Show all the circuits and waveform to the TA. Demonstration code (TA) : _____